

Probability Hardware Report in L^AT_EX

Shaik Armaan, cs22btech11051

1 COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE 0
COMPONENTS

2 METHOD

- 1) We connected the 555 timer circuit according to the figure 1

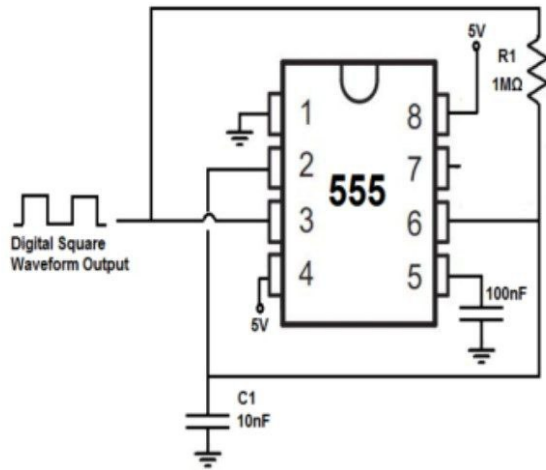


Fig. 1. Connection in 555 timer circuit

- 2) Then we connected Clock output of 555 timer circuit to the clock signal of D-Flip flops
- 3) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)

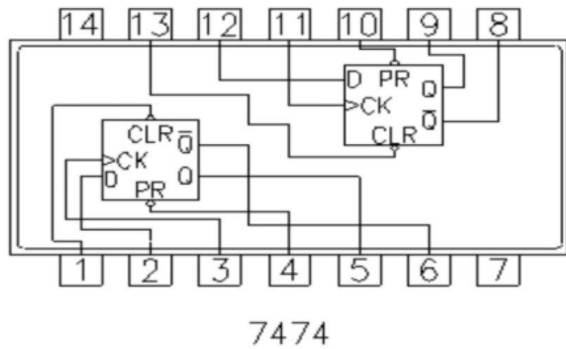


Fig. 3. Connection in 7474 IC

- 4) The out put of each D Flip Flop acts as the out put for the next Q and eventually the XOR gate will take in D_0 and D_3 as the inputs.
- 5) Then we connected XOR gate (7486 IC) according to the figure 5
- 6) then we connected the decoder (7447 IC) and connected its A,B,C,D with Q_0, Q_1, Q_2, Q_3 respectively as per the figure 6
- 7) Then we connected The seven segmented display and then connected it with the dceoder (7447 IC) according to the table 7 and the figure 7

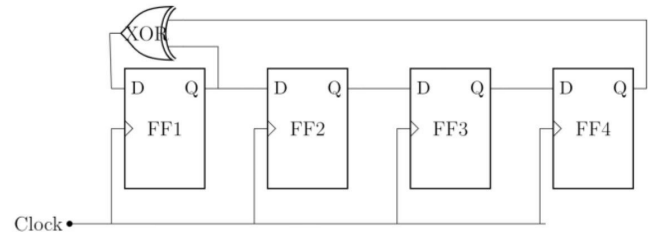


Fig. 5. Connection in XOR gate



Fig. 6. Connection in Decoder gate

- 8) We now connected the power source to our circuit and we get the numbers.

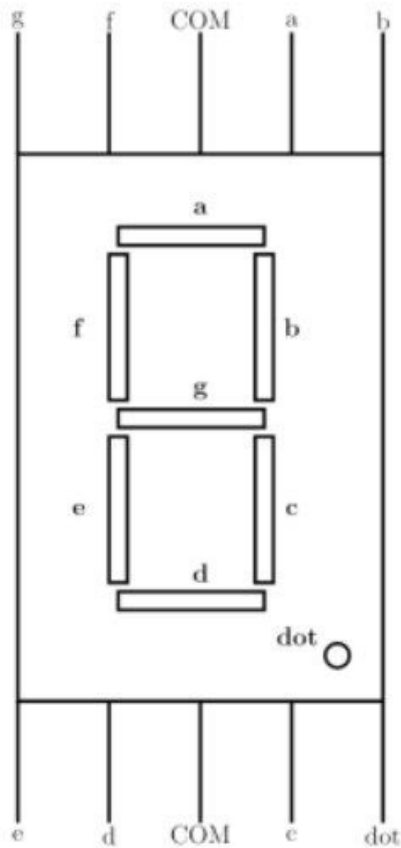


Fig. 7. Seven segmented display

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. 7. Connection of seven segmented display with decoder

3 OUTPUT

Output was changing digits on the seven segment display the output is shown in figure ??

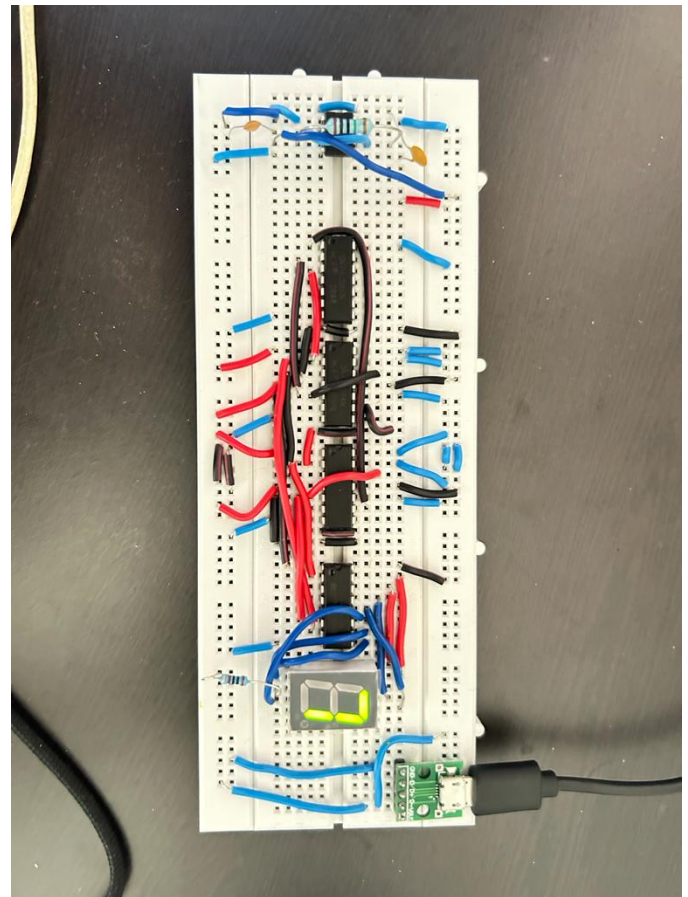


Fig. 8. output

4 CONCLUSION

- We basically are shifting outputs of D Flip Flops as the input to the next D Flip Flop which happens 4 times on our case.
- Finally the XOR gate takes in the value of D_0 and D_3 as the input and gives out the final number.
- The decoder IC 7447 basically decodes the output of the XOR gate and gives the voltage only to those segments that need to be turned on.
- And finally the seven segment display displays the random(not quite) number.

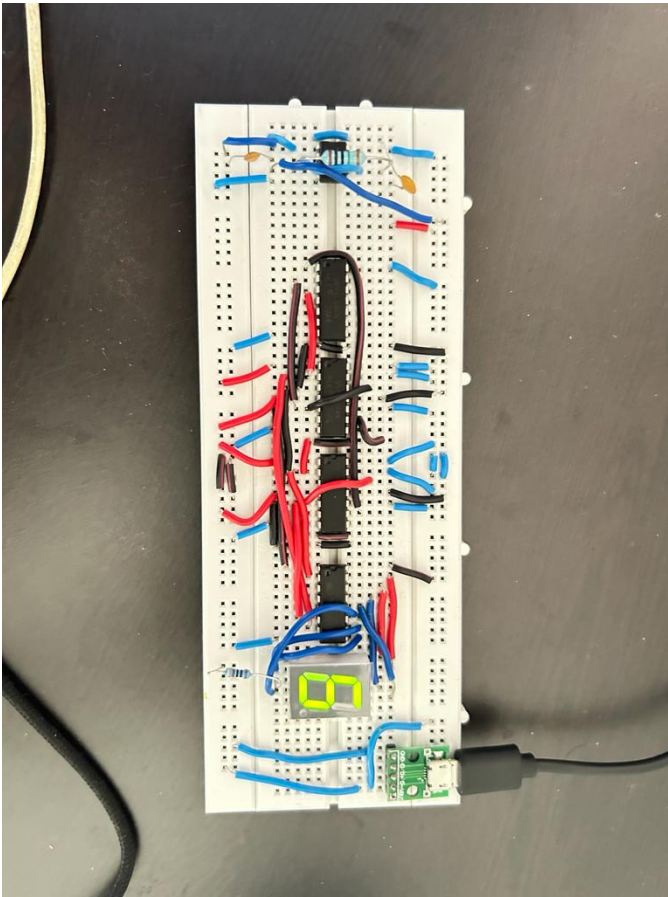


Fig. 8. output

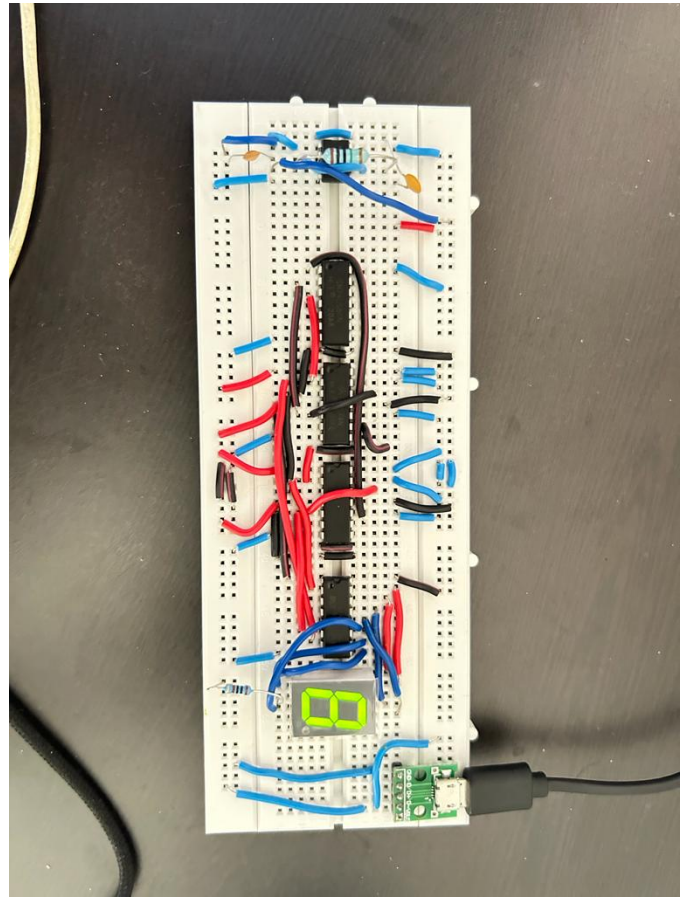


Fig. 8. output3

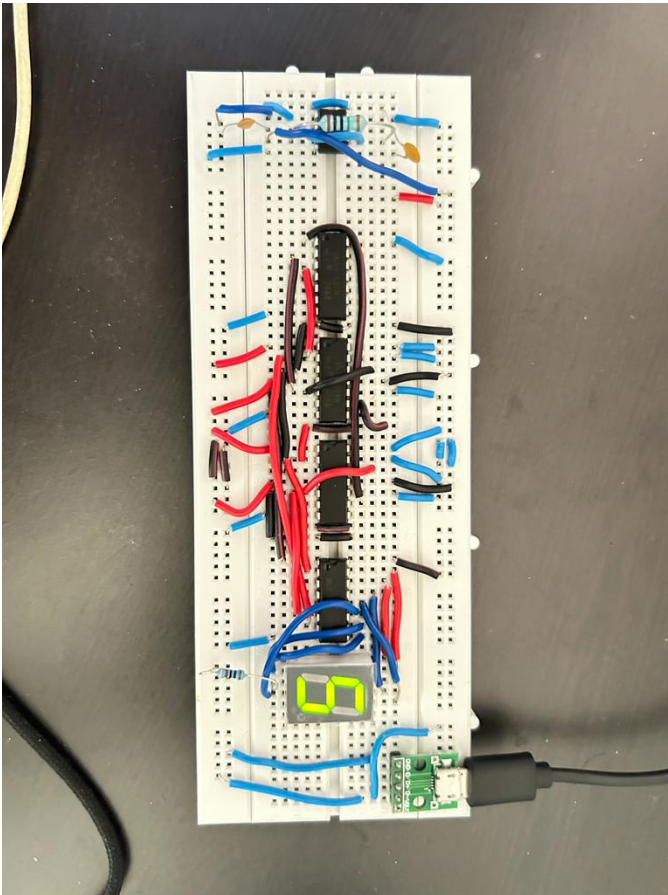


Fig. 8. output4